


# 1 Thevenin's Theorem

Thevenin's Theorem: Any resistive network or circuit can be represented as a voltage source in series with a source resistance. This helps predict how the circuit will respond to a change in load.

## 1.1 Thevenin Voltage

The Thevenin Voltage ( $V_{TH}$ ) of a circuit is the voltage present at the output terminal when the load is removed.


### 1.1.1 Example

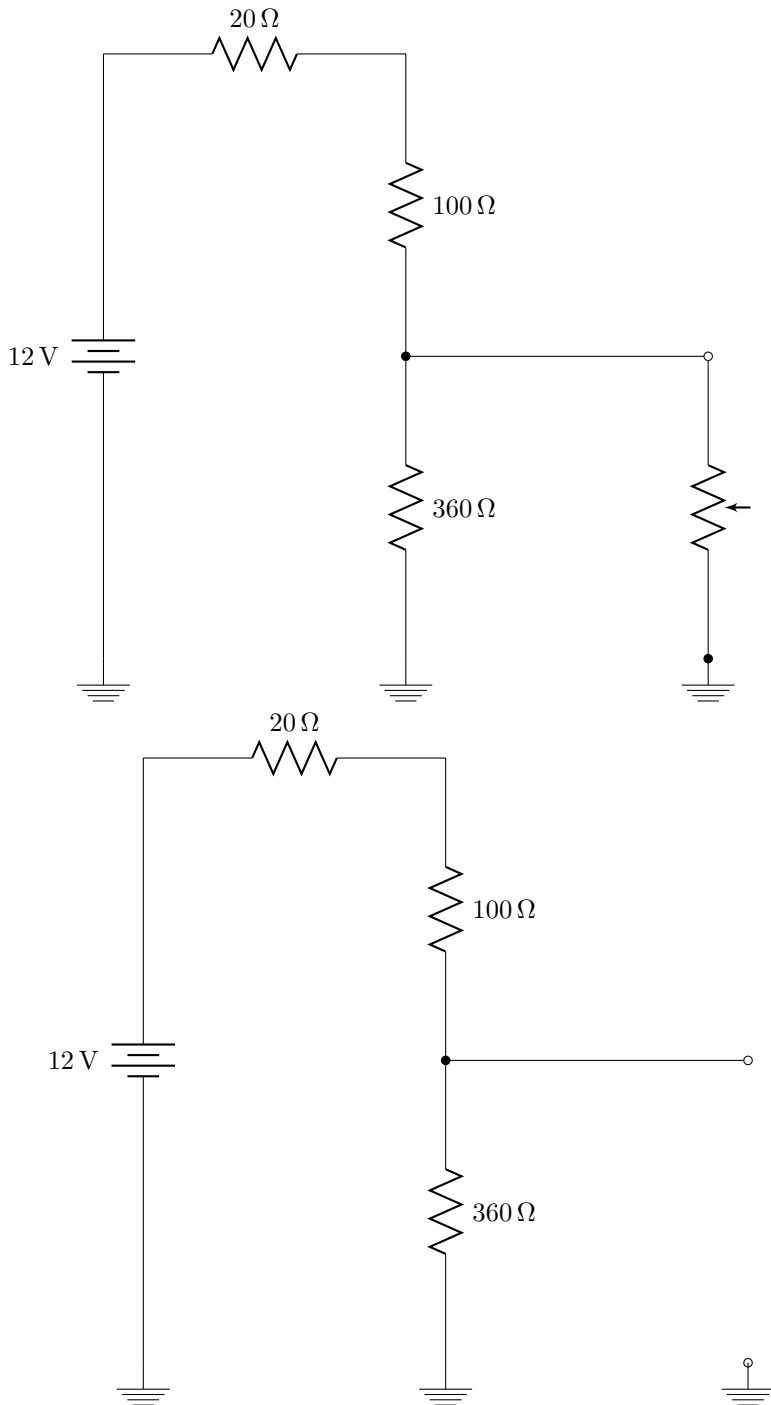

$$V_{TH} = V_S \frac{R_3}{R_T} = (12V) \frac{360\Omega}{480\Omega} = 9V$$
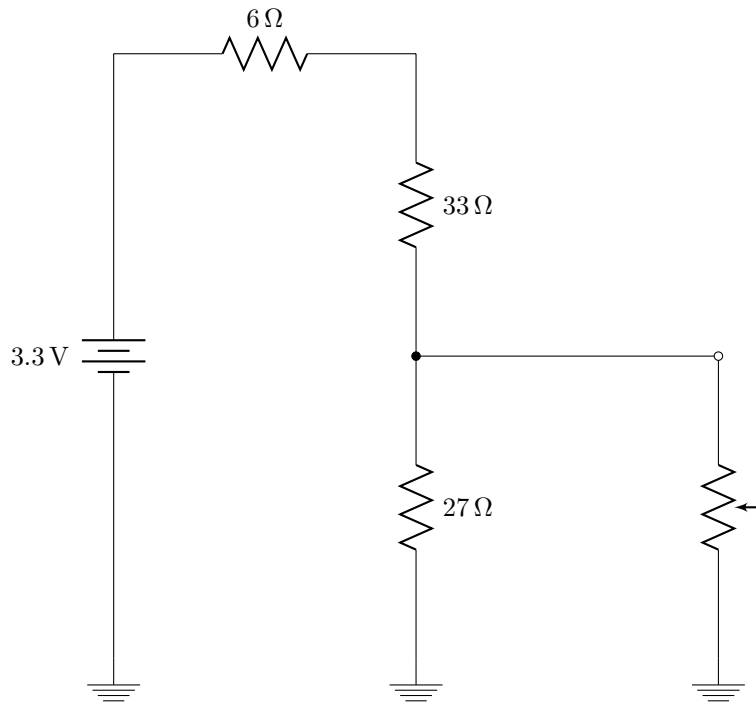
### 1.1.2 Problem

Find the Thevenin Voltage ( $V_{TH}$ ) of the circuit below:



## 1.2 Thevenin Resistance

The Thevenin Resistance ( $R_{TH}$ ) is the resistance measured across the output terminals when the load is removed. To determine this circuit we will also note the voltage source will be replaced by a wire.

### 1.2.1 Example